



In 0	In 1	X0	X1	X2
0	0	0	0	0
0	1	0	1	0
1	0	0	0	1
1	1	1	1	1

Wired OR

↓ 0 1 1 0